



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 70077

M.E./M.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019
First Semester
Applied Electronics
AP5151 – ADVANCED DIGITAL SYSTEM DESIGN
(Common to : M.E. VLSI Design, M.E. VLSI Design and Embedded Systems)
(Regulations 2017)

Time : Three Hours


Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

 1. State the two rules for state assignment in synchronous sequential circuits.
2. Draw the ASM chart for the following state diagram :



3. What are races and cycles in asynchronous sequential circuits ?
4. What are the two types of asynchronous sequential circuits ?
5. What is primitive D cube ?

70077

-2-



6. State the difference between PLA and PAL.
7. Mention any two advantages of Programmable Logic Devices.
8. Illustrate SRAM technology used in Xilinx FPGAs.
9. What is UDP in verilog ?
10. State the difference between task and function in verilog.

PART - B

(5×13=65 Marks)

11. a) Design a sequential network to convert BCD to Excess-3 Code. The input and output will be serial with the least significant bit first.

(OR)

- b) i) Design an iterative sequential parity-checking network which determines whether the number of ones in an n-bit word is even or odd. (5)
- ii) Draw the ASM chart for a binary divider and multiplier. (8)
12. a) i) In the following logic circuit assume that inputs b, c, d are provided with 1, 1 and 1 respectively. If the input a is changing from 0 to 1, analyse the hazard present at the output F. Also design a hazard-free logic. (8)

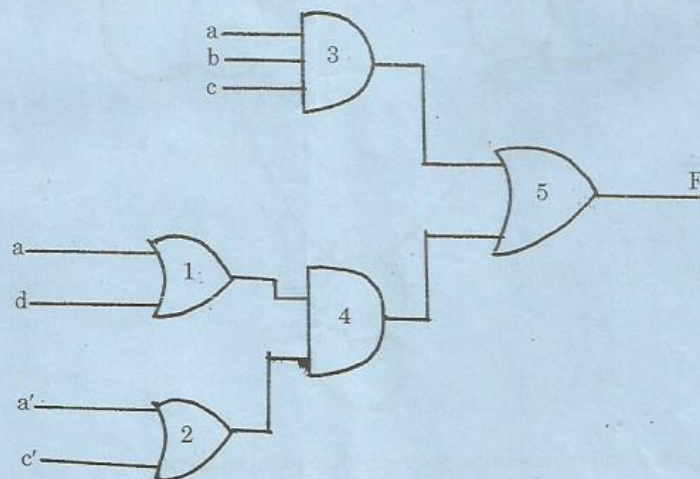


Fig.

- ii) What are dynamiz hazards ? Give example. (5)

(OR)



- b) For the given flow table :
- Find all critical races and tell why they are critical.
 - Find all non-critical races and
 - Find all cycles.
 - Draw a timing diagram showing what happens to Q_1 , Q_2 and Z when the network is started in state b and the input is changed from 01 to 00.

Q_1Q_2	X_1X_2				Z			
	00	01	11	10	00	01	11	10
00	(a)	c	b	c	0	0	0	0
01	c	(b)	(b)	d	1	0	1	0
11	d	(c)	b	d	0	1	0	0
10	c	(d)	b	(d)	1	1	0	0

13. a) For the logic circuit shown in Fig.
Derive the input test vector for the single stuck-at-fault in line h using.
- Fault-table method. (7)
 - Path-sensitization method. (6)

 


Fig.
(OR)

- b) Explain :
- D-algorithm. (8)
 - Built-in Self-Test Technique. (5)

70077

-4-



14. a) Design a 2-bit up-down counter and implement it using suitable PLA.
(OR)
- b) i) Explain the types of interconnects used in FPGAs. (5)
ii) With neat sketch, explain the Configurable Logic Block (CLB) of a Xilinx 4000 series FPGA. (8)
15. a) i) Design a full adder and write the verilog code using structural modeling. (5)
ii) Design a 2-bit parallel-in parallel-out shift register and write the verilog code to realize it using behavioral modeling. (8)
(OR)
- b) Design a multiplier and write the verilog code to realize it using behavioral modeling.

PART - C

(1×15=15 Marks)

16. a) Make a proper state assignment for the following table and give the expanded table.

	X_1X_2			
	00	01	11	10
a	①	7	②	10
b	5	③	9	4
c	⑤	⑥	8	10
d	1	⑦	⑧	4
e	1	3	⑨	⑩

Also make a one-hot assignment for the table and derive the next-state equations.

(OR)

- b) Design a simple microprocessor and write the verilog code to realize it.