



**PART – B (5 × 16 = 80 Marks)**

11. (a) Compare the various methods of biasing using BJT in terms of their stability factors. (16)

**OR**


- (b) With neat diagrams, explain two bias compensation techniques and state its advantages and disadvantages. (16)

12. (a) What are the changes in the a.c characteristics of a common emitter amplifier when an emitter resistor and an emitter bypass capacitor are incorporated in the design? Explain with necessary equations. (16)

**OR**

- (b) (i) Calculate the small signal voltage gain of an emitter follower circuit.  
Given  $\beta = 100$ ,  $V_{BE(on)} = 0.7V$ ,  $V_A = 80 V$ ,  $I_{CQ} = 0.793 mA$ ,  $V_{CEQ} = 3.4 V$ . (8)  
(ii) Draw and explain the operation of a darlington amplifier. (8)

13. (a) Design a JFET source follower circuit (Figure 13(a)) with a specified small signal voltage gain given  $I_{DSS} = 12mA$ ,  $V_p = -4V$ ,  $\lambda = 0.01 V^{-1}$ . Determine  $R_s$  and  $I_{DQ}$  such that the small signal voltage gain is at least  $A_v = V_o/V_i = 0.90$ . (16)

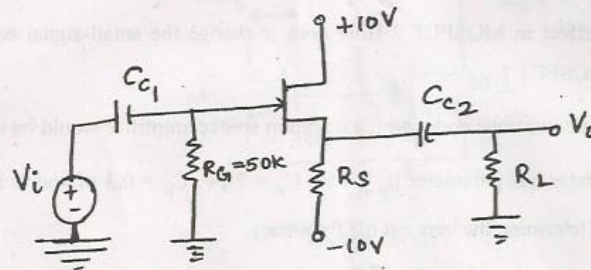

**Figure 13(a)**

**OR**

- (b) Determine the small signal voltage gain of a common source circuit (Figure 13(b)) containing a source resistor. The transistor parameters are  $V_{TN} = 0.8 \text{ V}$ ,  $K_n = 1 \text{ mA/V}^2$  and  $\lambda = 0$ . (16)

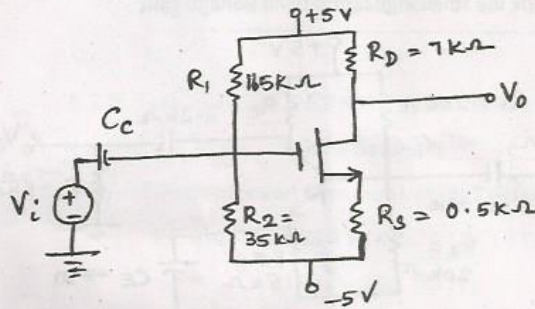


Figure 13(b)

14. (a) Determine the 3 dB frequencies and mid band gain of a cascade circuit. For the Figure 14(a) the parameters are  $V^+ = 10 \text{ V}$ ,  $V^- = -10 \text{ V}$ ,  $R_s = 0.1 \text{ k}\Omega$ ,  $R_1 = 42.5 \text{ k}\Omega$ ,  $R_2 = 20.5 \text{ k}\Omega$ ,  $R_3 = 28.3 \text{ k}\Omega$ ,  $R_E = 5.4 \text{ k}\Omega$ ,  $R_C = 5 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  $C_L = 0$ . The transistor parameters are  $\beta = 150$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ ,  $V_A = \infty$ ,  $C_\pi = 35 \text{ pF}$  and  $C_\mu = 4 \text{ pF}$ . (16)

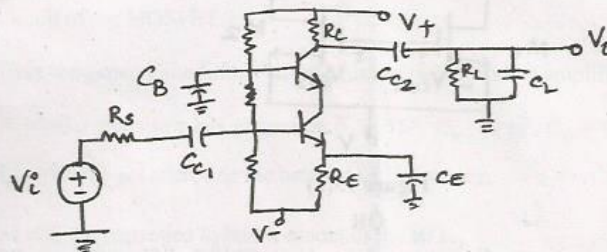


Figure 14(a)

OR

- (b) The transistor in the figure. 14(b) has parameters  $\beta = 125$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ ,  $V_A = 200 \text{ V}$ ,  $C_\pi = 24 \text{ pF}$  and  $C_\mu = 3 \text{ pF}$ .
- Calculate the miller capacitor
  - Determine the upper 3 dB frequency
  - Determine the small signal mid band voltage gain
- (16)

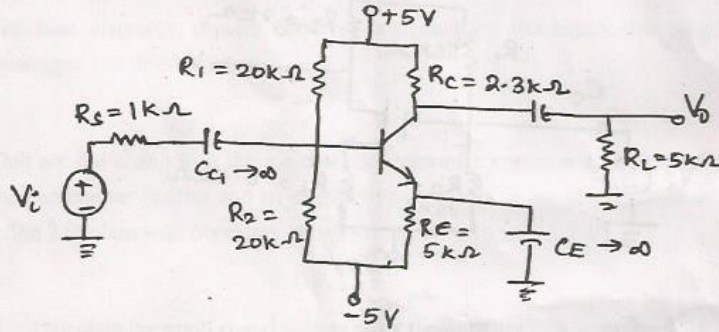


Figure. 14(b)

15. (a) For the circuit shown in the figure. 15(a) Let  $V^+ = 10 \text{ V}$ , and  $V^- = 0$  and the transistor parameters are  $V_{TN} = 2 \text{ V}$ ,  $\frac{1}{2} \mu_n C_{ox} = 20 \mu\text{A/V}^2$  and  $\lambda = 0$ . Design the circuit such that  $I_{ref} = 0.5 \text{ mA}$  and  $I_o = 0.2 \text{ mA}$  and  $M_2$  remains biased in the saturation region for  $V_{DS2} \geq 1 \text{ V}$ .
- (16)

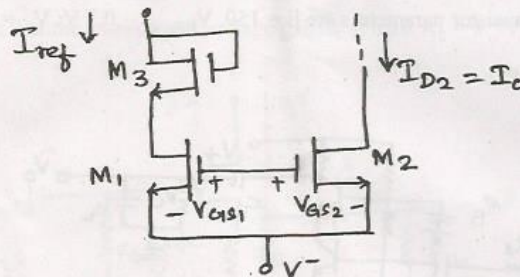


Figure 15(a)

OR

- (b) With the necessary diagram explain about CMOS differential amplifier and derive the CMRR.
- (16)