

PART B — (5 × 16 = 80 marks)

11. (a) (i) Explain in detail about the reflection on a line not terminated by its characteristic impedance Z_0 . (8)
- (ii) Derive the condition for minimum attenuation in a distortionless line. (8)

Or

- (b) A Communication line has $L = 3.67$ mH/km, $G = 0.08 \times 10^{-6}$ mhos/km, $C = 0.0083$ μ F/km and $R = 10.4$ ohms/km. Determine the characteristic impedance, propagation constant, phase constant, velocity of propagation, sending end current and receiving end current for given frequency $f = 1000$ HZ, Sending end voltage is 1 volt and transmission line length is 100 kilometers. (16)
12. (a) (i) Derive an expression for the input impedance of a dissipationless line and also find the input impedance is maximum and minimum at a distance 's'. (8)
- (ii) Find the sending end line impedance for a HF line having characteristic impedance of 50Ω . The line is of length (1.185λ) and is terminated in a load of $(110 + j80) \Omega$. (8)

Or

- (b) (i) Describe an experimental set up for the determination of VSWR of an RF transmission. (8)
- (ii) Briefly explain on :
- (1) Standing Waves
- (2) Reflection loss. (4 + 4)
13. (a) (i) Determine length and location of a single short circuited stub to produce an impedance match on a transmission line with characteristic impedance of 600Ω and terminated in 180Ω . (8)
- (ii) Explain the operation of quarter wave transformer and mention its important applications. (8)

Or

- (b) (i) Find the sending end impedance of a line with negligible losses when characteristic impedance is 55Ω and the load impedance is $115 + j75 \Omega$ length of the line is 1.183 wave length by using smith chart. (10)
- (ii) Explain the significance of smith chart and its application in a transmission lines. (6)

14. (a) What is m-Derived filter? Draw a m-Derived T-section and π -section low pass filter and explain the analysis of m-Derived low pass filter with respect to attenuation, phase shift and characteristic impedance with frequency profile respectively. (16)

Or

- (b) What is composite filter? Design a constant-K-low pass filter (T-section and π -section) and having cut-off at which 2.5 KHz and design resistance R_0 is 700Ω . Also find the frequency at which this filter produces attenuation of 19.1 dB. Find its characteristic impedances and phase constant at pass band and stop or attenuation band. (2 + 14)
15. (a) Derive an expression for the transmission of TE waves between parallel perfectly conducting planes for the field components. (16)

Or

- (b) (i) Write a brief note on circular cavity resonator and its application.(8)
- (ii) A TE_{11} wave is propagating through a circular waveguide. The diameter of the guide is 10 cm and the guide is air-filled. Given $X_{11} = 1.842$.
- (1) Find the cut-off frequency. (3)
- (2) Find the wavelength λ_g in the guide for a frequency of 3 GHz. (2)
- (3) Determine the wave impedance in the guide. (3)