## www.binils.com Anna University | Polytechnic | Schools

Reg. No.:						

## Question Paper Code: X10392

## B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2020

Third Semester
Mechanical Engineering

EE 8353 – ELECTRICAL DRIVES AND CONTROLS

(Common to Manufacturing Engineering/Mechanical and Automation Engineering)

(Regulations 2017)

Time: Three Hours

Maximum: 100 Marks

Answer ALL questions

PART – A (10×2=20 Marks)

- 1. What are the advantages of electrical drive?
- 2. What are the requirements of an electric drive?
- 3. What are the different methods of braking applied to the induction motor?
- 4. What is the significance of DC series motor?
- 5. State the purpose of rotor resistance starter.
- 6. State the need of starters in electric motors.
- 7. What are the methods involved in armature voltage control?
- 8. What is a chopper?
- 9. What is meant by V/F control?
- 10. What is the advantage of induction motor over a DC motor?

PART – B

 $(5\times13=65 \text{ Marks})$ 

- 11. a) i) Discuss the various factors which decide the choice of an electric drive. (7)
  - ii) Briefly explain the heating and cooling curves of an electric drive. (6)

b) Discuss the different classes of duty cycle.

(OR)

## www.binils.com Anna University | Polytechnic | Schools

X10392

12. a) Explain the speed torque characteristics of three phase induction motor with neat diagrams.

(OR)

- b) Explain various methods of braking used for shunt and series motors.
- 13. a) Explain auto transformer and star-delta starters for AC motors.

(OR)

- b) With neat diagram, explain the working of DC motor starter using time delay relays.
- 14. a) Discuss the ward-leonard speed control system with a neat diagram. Also mention its advantages and disadvantages.

(OR)

- b) Explain the speed control of dc shunt motor using fully controlled rectifiers.
- 15. a) Explain the slip power recovery control of slip ring induction motor in detail.

(OR)

b) Explain the pole changing method of speed control for a squirrel cage Induction motor.

PART – C (1×15=15 Marks)

16. a) Analyze the speed control of a three phase induction motor using three phase bridge inverter.

(OR)

b) Analyze the theory of three point and four point starter in detail.

\_\_\_\_\_