
#### 3.7 TYPES OF DC MOTOR:

1. Separately excited DC

motor 2.Self excited dc motor

- Series motor
- Shunt motor
- Compound motor
  - 1. Long shunt compound motor
  - 2. Short shunt compound motor

#### SEPARATELY EXCITED DC MOTOR:

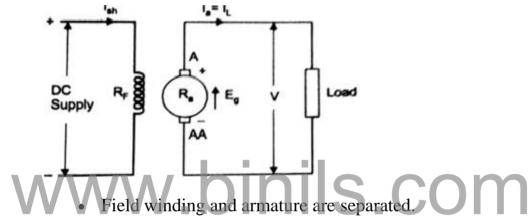


- Field winding is excited by a separate DC source-separately excited dc motor.
- Ia=I1
- E<sub>b</sub> =V-Ia Ra-Vbrush

#### DC SERIES MOTOR:

- Field winding is connected in series with armature.
- Less number of turns.
- Rse –resistance of series field winding-small.
- Il=line current
- Ia=series field
- $V=E_b + Ia Ra + IscRsc+V brush.$
- $V = E_b + (Ra + Rse)$ .
- Φ α Ise α Ia

#### DC SHUNT MOTOR:

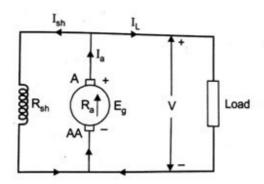

- Field winding is connected across the armature.
- More number of turns with less cross sectional area.
- Rsh is the shunt field winding
- Ra is the armature resistance.
- Ra is small, Rsh is large.
- Voltage v=voltage across the armature and field winding.
- Il is the line current, divided into two paths
- Field winding 1.
- .binils.com Armature winding 2.
- Il = Ia + Ish
- Ia = armature current
- Ish =shunt field current
- Ish = V / Rsh
- $V = E_b + Ia Ra + V brush$
- Φ α Ish
- Input is constant, so flux is constant.
- Also known as constant flux motor.


#### DC COMPOUND MOTOR:

#### 1. LONG SHUNT:

- Shunt field winding is connected to both the armature and the field winding.
- Il = Isc + Ish
- Ise = Ia
- I1 = Ia + Ish
- Ish = V/Rsh

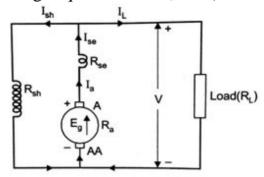**BE3251 BASIC ELECTRICAL AND ELECTRONICS ENGINEERING** 


• Voltage equation  $V = E_b + Ia(Ra + Rse) + V$  brush



# www.binils.com

**BE3251 BASIC ELECTRICAL AND ELECTRONICS ENGINEERING** 

#### 2. SHORT SHUNT:

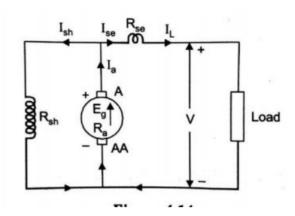

- Shunt field winding is connected across armature and series field winding is connected in series.
- I1 = Ise
- inils.com I1 = Ia + IshIl = Ise = Ia + Ish
  - Voltage drop= v -Il Rse
  - $V = E_b + Ia Ra + V brush$
  - Ish = V- IlRse/ Rsh.